

Electronics 2

FINAL

Professor Cliver ENT-2156

(EEET-221 36907)

Name: _____

Class time (ex. 1 p.m.): _____

1. If $I_{B+} = 214 \text{ nA}$ and $I_{B-} = 188 \text{ nA}$ determine the input offset current (I_{OS})
 - (a) 26 nA
 - (b) 214 nA
 - (c) 402 nA
 - (d) 201.00 nA

2. If $V_{IN1} = 7V$, $V_{IN2} = 1V$, $V_{O(SAT)} = \pm 15V$ and, $R_L = 5K\Omega$ in figure 1, determine the output current I_L of the comparator (the current through R_L).
 - (a) 1.20 mA
 - (b) 0.80 mA
 - (c) -3.00 mA
 - (d) 3.00 mA

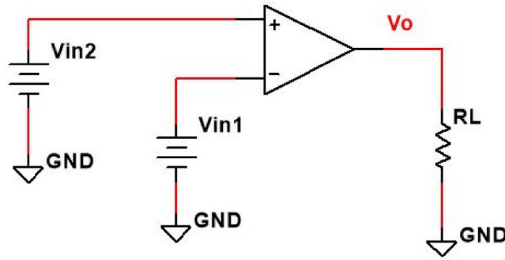


Figure 1: Comparitor

3. An op-amp has a slew-rate of $4\frac{V}{\mu s}$ and is configured as a non-inverting amplifier $R_F = 9.9K\Omega$ and $R_I = 3.2K\Omega$. If a 8.00mV peak sine wave is applied to the non-inverting input, determine the slew rate limiting frequency (maximum sine wave frequency).
- (a) 19.4 MHz
 - (b) 79.6 MHz
 - (c) 122.1 MHz
 - (d) 246.2 MHz
4. An op-amp has a unity gain frequency of 4 MHz and is configured as a non-inverting amplifier $R_f = 9.8K\Omega$ and $R_i = 3.2K\Omega$. Calculate the rise time (t_{CL}) associated with the amplifier.
- (a) 4.00 ns
 - (b) 1015.63 ns
 - (c) 0.98 ns
 - (d) 355.47 ns

5. Find V_- (voltage at the inverting input) if $V_{in}=1.06V$, $R_i=62K\Omega$, $R_f=18K\Omega$ and $R_L=134K\Omega$ in Figure 2.

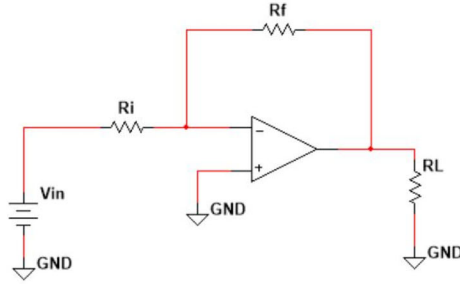


Figure 2: Inverting Amplifier

6. Find I_f (current in R_f) if $V_{in}=0.20V$, $R_i=2K\Omega$, $R_f=5K\Omega$ and $R_L=133K\Omega$ in Figure 3.

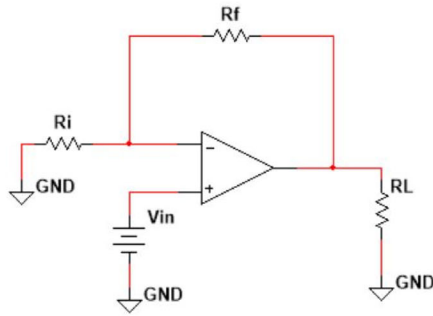


Figure 3: Non-Inverting Amplifier

7. Find V_- (voltage at the inverting input) if $V_{in}=0.22V$, $R_i=40K\Omega$, $R_f=12K\Omega$ and $R_L=141K\Omega$ in Figure 4.

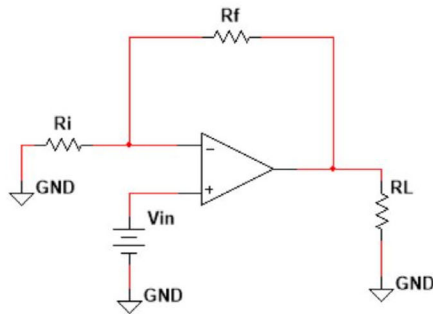


Figure 4: Non-Inverting Amplifier

8. Find the noise gain if $V_{in}=0.54V$, $R_i=14K\Omega$, $R_f=17K\Omega$ and $R_L=151K\Omega$ in Figure 5.

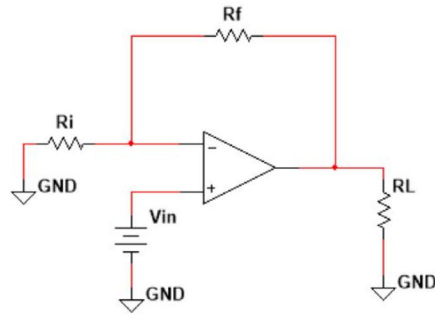


Figure 5: Amplifier

9. Find I_L (current in R_L) if $V_{in}=0.58V$, $R_i=65K\Omega$, $R_f=21K\Omega$ and $R_L=139K\Omega$ in Figure 6.

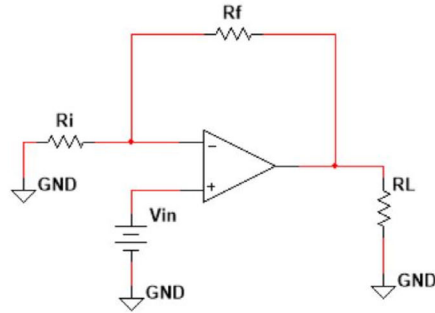


Figure 6: Non-Inverting Amplifier

10. Find V_L if $V_{io}=4\text{mV}$, $R_i=2\text{K}\Omega$, $R_c=2\text{K}\Omega$ and $R_f=153\text{K}\Omega$ in Figure 7.

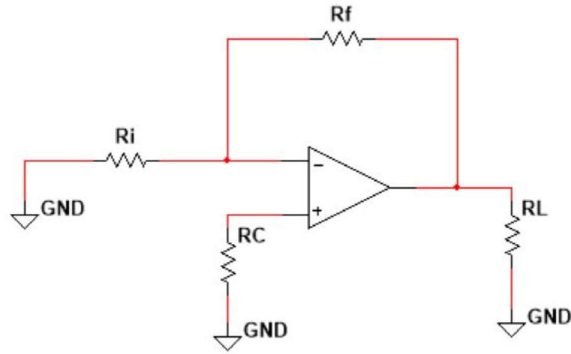


Figure 7: Input Offset Voltage

11. Find the closed loop 3-dB bandwidth for a non-inverting amplifier if the unity gain frequency $B=3\text{MHz}$, $R_i=2\text{K}\Omega$ and $R_f=177\text{K}\Omega$.

The problems on this page both use the same figure.

12. Sketch the input-output characteristic curve given $R_1 = 9.3K\Omega$, $R_2 = 3.9K\Omega$ and $V_{O(SAT)} = \pm 12V$ in Figure 8.

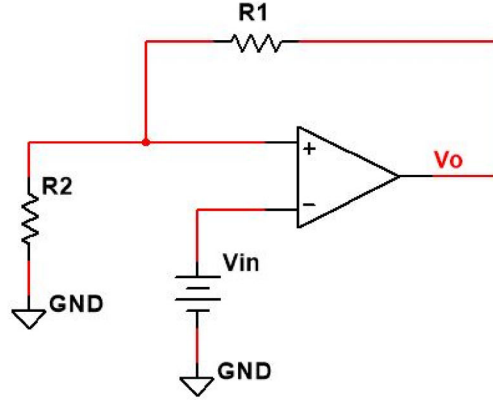


Figure 8: Inverting Schmitt Trigger

13. Sketch the output curve given the input curve in Figure 9 and $R_1 = 9.5K\Omega$, $R_2 = 3.5K\Omega$ and $V_{O(SAT)} = \pm 13V$ in Figure 8.


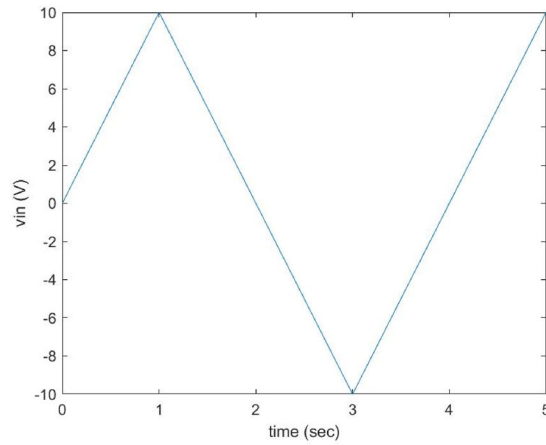



Figure 9: Input Output Curve

The problems on this page both use the same figure.

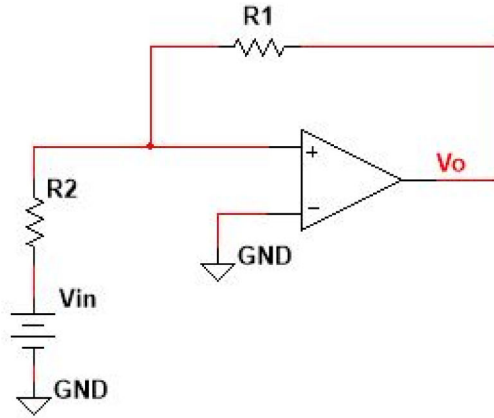14. Sketch the input-output characteristic curve given $R_1 = 9.7K\Omega$, $R_2 = 3.2K\Omega$ and $V_{O(SAT)} = \pm 14V$.




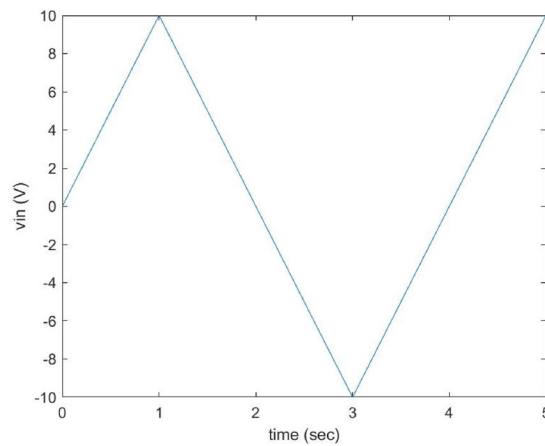15. Sketch the output curve given the input curve and $R_1 = 8.1K\Omega$, $R_2 = 4.7K\Omega$ and $V_{O(SAT)} = \pm 14V$.



The problems on this page both use the same figure.

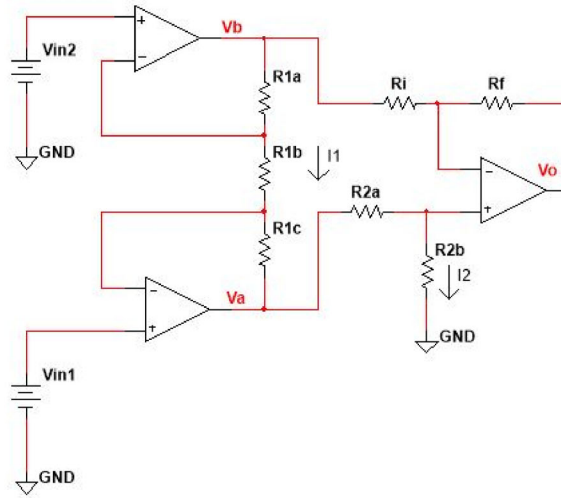16. Determine the current I_1 given all resistors are $= 2.0K\Omega$ except R_{1b} that is $= 4.6K\Omega$ and $V_{in1} = 6V$ and $V_{in2} = 13V$.



17. Using the same circuit and values, determine I_2 .

18. A 4-pole high-pass Butterworth filter has a 3-dB cutoff of 6 MHz. Use figure 8-7 to determine the decibel response at 2 MHz.


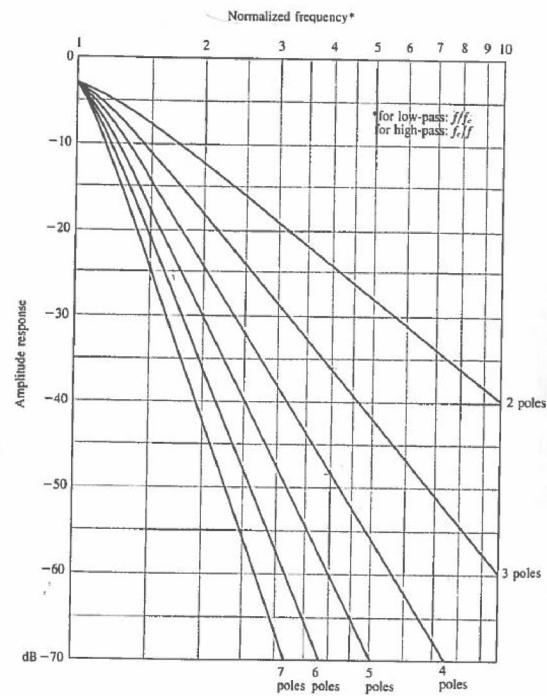


FIGURE 8-7
Stop-band amplitude response of Butterworth filters.

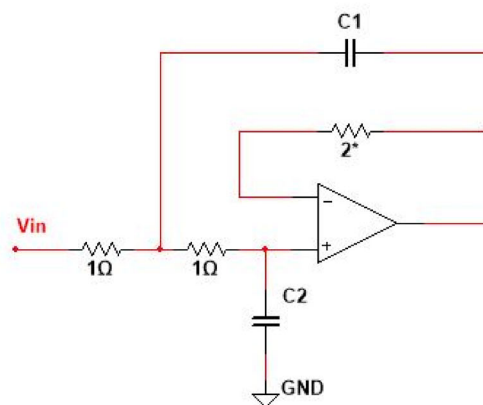19. Design a two-pole low-pass Butterworth active filter using the unity-gain amplifier (below) to achieve a 3dB frequency of 6 KHz. Select the two filter resistances at $12\text{K}\Omega$ each. Starting values for C_1 and C_2 are 1.414 and 0.7071, respectively.



20. What is the minimum order needed for a high-pass filter that has:

- (a) relative amplitude ≤ 0.100 dB for $f \geq 4.0$ KHz.
- (b) relative amplitude ≥ 30.0 dB for $f \leq 0.600$ KHz.

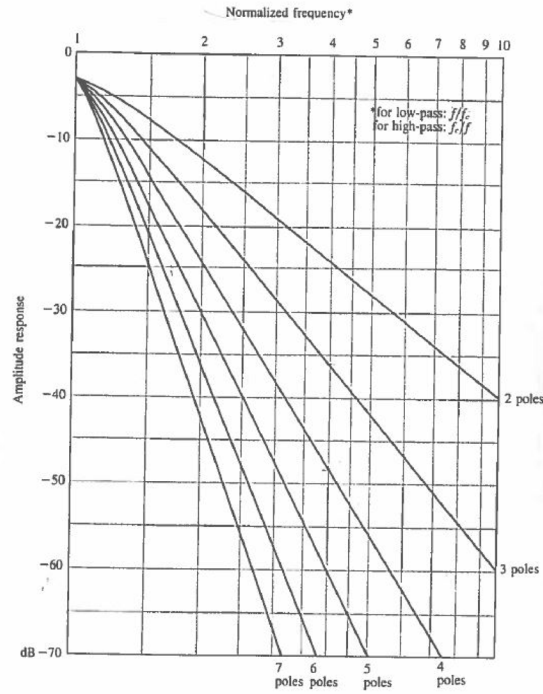


FIGURE 8-7
Stop-band amplitude response of Butterworth filters.

TABLE 8-1
Data for determining pass-band relative amplitude response for
Butterworth filters

Amplitude Response (dB)	f/f_c for Low-Pass f_c/f for High-Pass					
	$n = 2$	$n = 3$	$n = 4$	$n = 5$	$n = 6$	$n = 7$
-0.01	0.219	0.363	0.468	0.545	0.603	0.648
-0.02	0.261	0.408	0.511	0.584	0.639	0.681
-0.05	0.328	0.476	0.573	0.640	0.690	0.727
-0.1	0.391	0.534	0.625	0.687	0.731	0.764
-0.2	0.466	0.601	0.683	0.737	0.775	0.804
-0.5	0.591	0.704	0.769	0.810	0.839	0.860
-1	0.713	0.798	0.845	0.874	0.894	0.908
-2	0.875	0.914	0.935	0.948	0.956	0.962
-3.01	1	1	1	1	1	1

21. What has been the most confusing point so far in the class?

This image shows a blank sheet of white paper with horizontal ruling lines. The lines are evenly spaced and extend across the width of the page. There are no margins, text, or other markings on the paper.