

EEET-221 Final Exam

Skyler MacDougall

1. If $I_{b+} = 214\text{nA}$ and $I_{b-} = 188\text{nA}$, determine I_{os} .
 1. 26nA
 2. 214nA
 3. 402nA
 4. 201.00nA
2. If $V_{in1} = 7\text{V}$, $V_{in2} = 1\text{V}$, $V_{O_{SAT}} = \pm 15\text{V}$, $R_L = 5\text{k}\Omega$ in figure 1, determine the output current I_L of the comparator (the current through R_L).


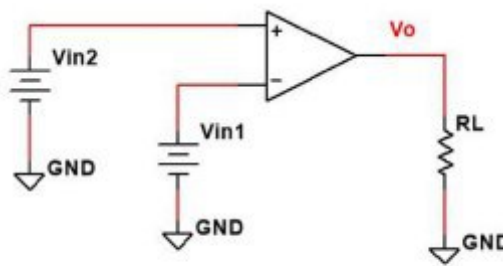


Figure 1: Comparitor

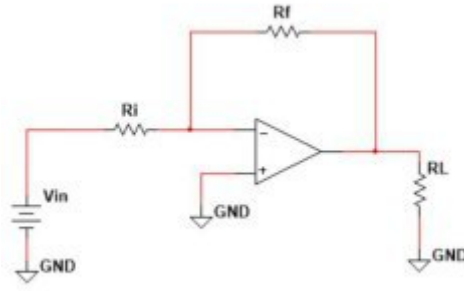1. 1.20mA
 2. 0.80mA
 3. -3.00mA
 4. 3.00mA
3. An op-amp has a slew rate of $4\frac{\text{V}}{\mu\text{s}}$ and is configured as a non-inverting amplifier, where $R_f = 9.9\text{k}\Omega$, $R_i = 3.2\text{k}\Omega$. If a 8.00mV peak sine wave is applied to the non-inverting input, determine the slew rate limiting frequency.
 1. 19.4MHz
 2. 79.6MHz
 3. 122.1MHz
 4. 246.2MHz
 4. An op-amp has a unity gain frequency of 4MHz and is configured as a non-inverting amplifier where $R_f = 9.8\text{k}\Omega$, $R_i = 3.2\text{k}\Omega$. Calculate the rise time (t_{CL}) associated with the amplifier.
 1. 4.00ns
 2. 1015.63ns
 3. 0.98ns
 4. 355.47ns
 5. Find the voltage at the inverting input if:

$$\begin{aligned} V_{in} &= 1.06\text{V} \\ R_i &= 62\text{k}\Omega \\ R_f &= 18\text{k}\Omega \\ R_L &= 134\text{k}\Omega \end{aligned} \quad (1)$$



$$V_- = V_+ \quad (2)$$

$$\therefore$$

$$V_- = 0V$$

6. Find the current in R_f if, using the diagram in question 5:

$$V_{in} = 0.20V \quad (3)$$

$$R_i = 2k\Omega$$

$$R_f = 5k\Omega$$

$$R_L = 133k\Omega$$

$$V_o = \left(1 + \frac{R_f}{R_i}\right)V_i \quad (4)$$

$$V_o = 700mV$$

$$I_f = \frac{0.2V - 0.7V}{5k\Omega}$$

$$\boxed{I_f = -100mA}$$

7. Find the voltage at the inverting input, given the diagram in question 5 and:

$$V_{in} = 0.22V \quad (5)$$

$$R_i = 40k\Omega$$

$$R_f = 12k\Omega$$

$$R_L = 141k\Omega$$

$$V_- = V_+ \quad (6)$$

$$\boxed{V_- = 0.22V}$$

8. Find the noise gain given the diagram in question 5 and:

$$V_{in} = 0.54V \quad (7)$$

$$R_i = 14k\Omega$$

$$R_f = 17k\Omega$$

$$R_L = 151k\Omega$$

$$k_n = 1 + \frac{R_f}{R_i} = 1 + \frac{17k\Omega}{14k\Omega} \quad (8)$$

$$\boxed{k_n = 2.2143}$$

9. Find the current in R_L given the diagram in question 5 and:

$$V_{in} = 0.58V \quad (9)$$

$$R_i = 65k\Omega$$

$$R_f = 21k\Omega$$

$$R_L = 139k\Omega$$

$$V_o = (1 + \frac{R_f}{R_i})V_i = (1 + \frac{21k\Omega}{65k\Omega})0.58V \quad (10)$$

$$V_o = 767.38mV$$

$$I_L = \frac{V_o}{R_L} = \frac{767.38mV}{139k\Omega}$$

$$\boxed{I_L = 5.52\mu A}$$


10. Find V_L given:

$$V_{io} = 4mV \quad (11)$$

$$R_i = 2k\Omega$$

$$R_c = 2k\Omega$$

$$R_f = 153k\Omega$$

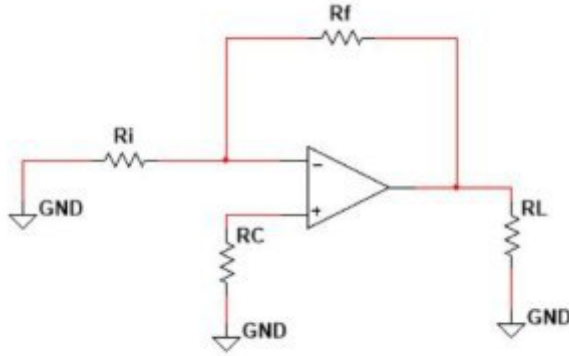

$$V_L = V_{io}(1 + \frac{R_f}{R_i}) = 4mV(1 + \frac{153k\Omega}{2k\Omega}) \quad (12)$$

$$\boxed{V_L = 310mV}$$

11. Find the closed loop 3dB bandwidth for a non-inverting amplifier if given the following:

$$B = 3MHz \quad (13)$$

$$R_i = 2k\Omega$$

$$R_f = 177k\Omega$$

$$BW = \frac{B}{k_n} = \frac{3MHz}{1 + \frac{R_f}{R_i}} = \frac{3MHz}{1 + \frac{177k\Omega}{2k\Omega}} = \frac{3MHz}{89.5} \quad (14)$$



$$\boxed{BW = 33.52kHz}$$

12. Sketch the input-output characteristic curve, given:

$$R_1 = 9.3k\Omega \quad (15)$$

$$R_2 = 3.9k\Omega$$

$$V_{O_{SAT}} = \pm 12V$$

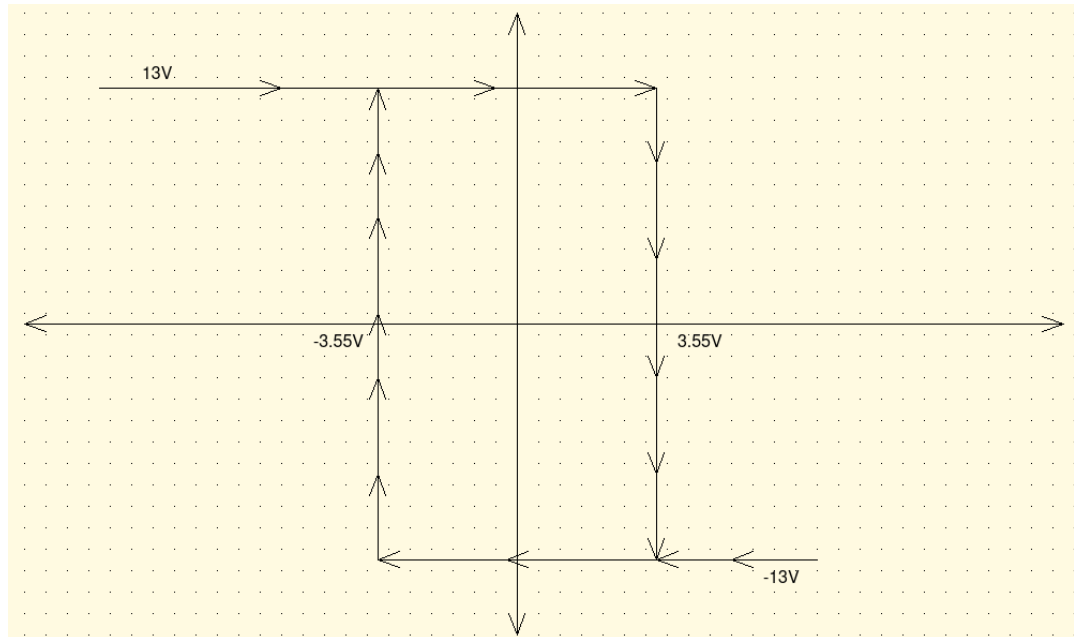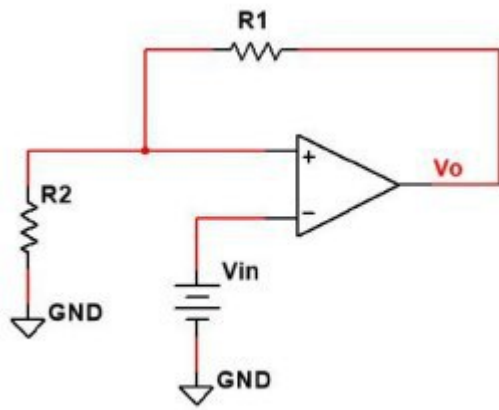



13. Sketch the output curve given the diagram in question 12 and:

$$R_1 = 9.5k\Omega$$

$$R_2 = 3.5k\Omega$$

$$V_{O_{SAT}} = \pm 13V$$

(16)

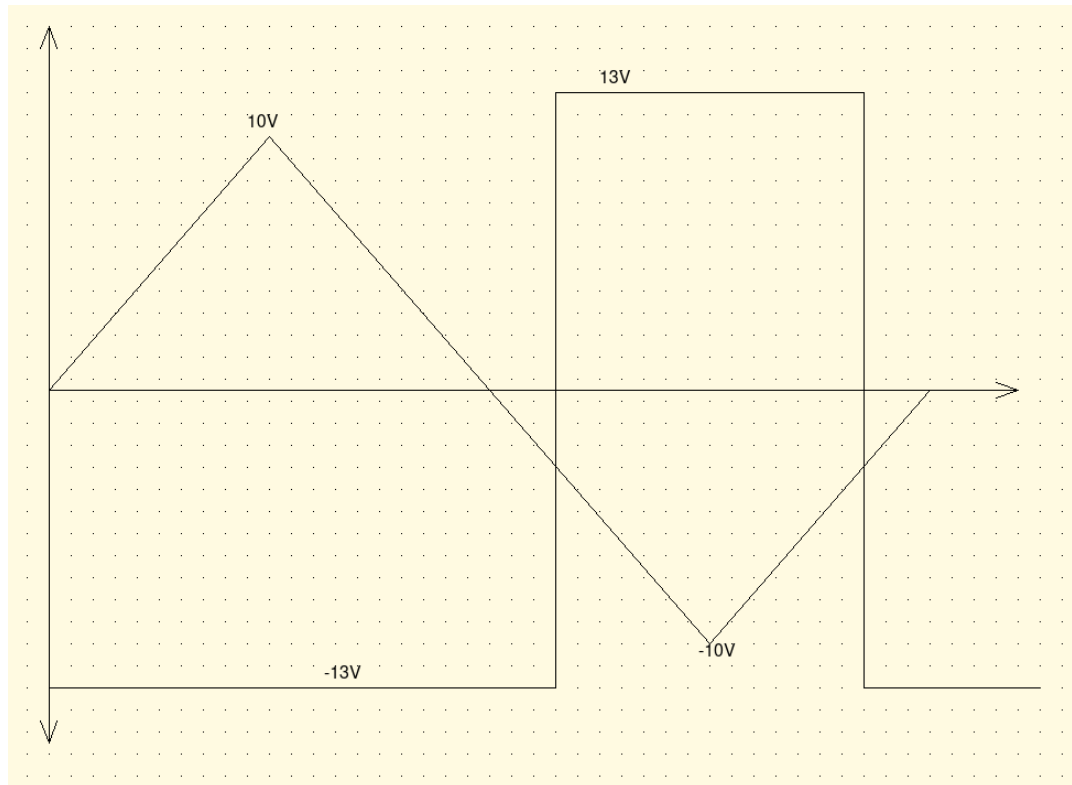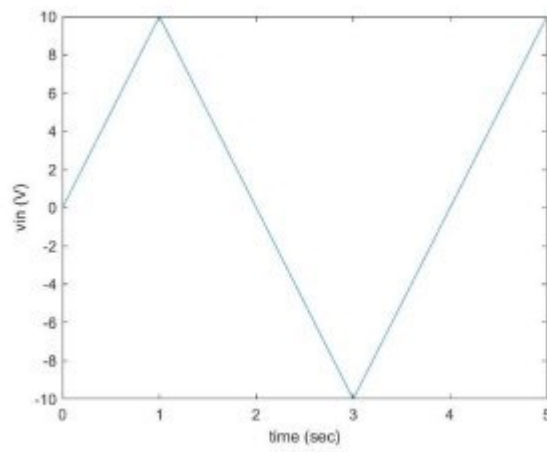



14. Sketch the input-output characteristic curve given:

$$R_1 = 9.7k\Omega \quad (17)$$

$$R_2 = 3.2k\Omega$$

$$V_{O_{SAT}} = \pm 14V$$

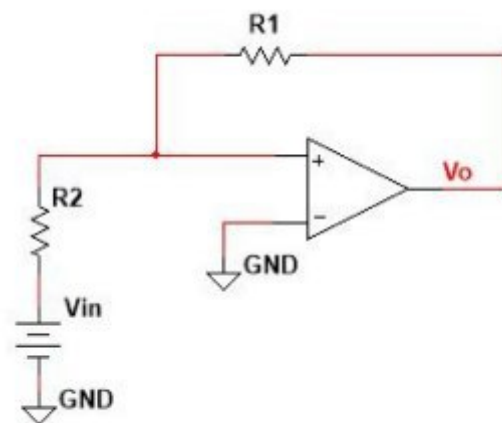


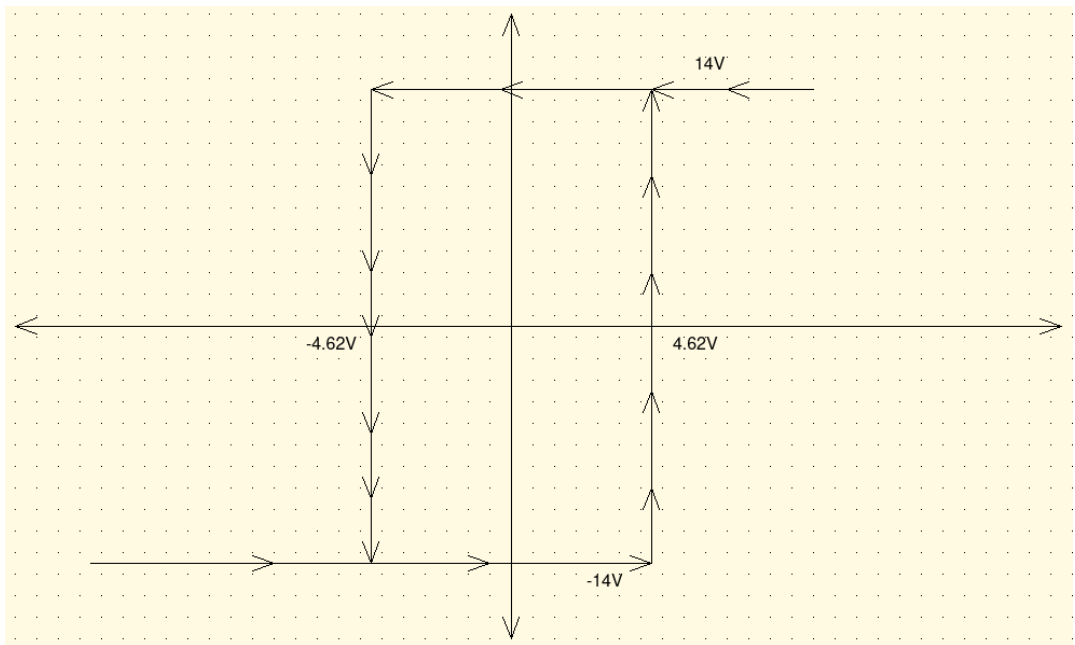


15. Sketch the output curve given the diagram in question 14 and:


$$R_1 = 8.1k\Omega \quad (18)$$

$$R_2 = 4.7k\Omega$$

$$V_{O_{SAT}} = \pm 14V$$

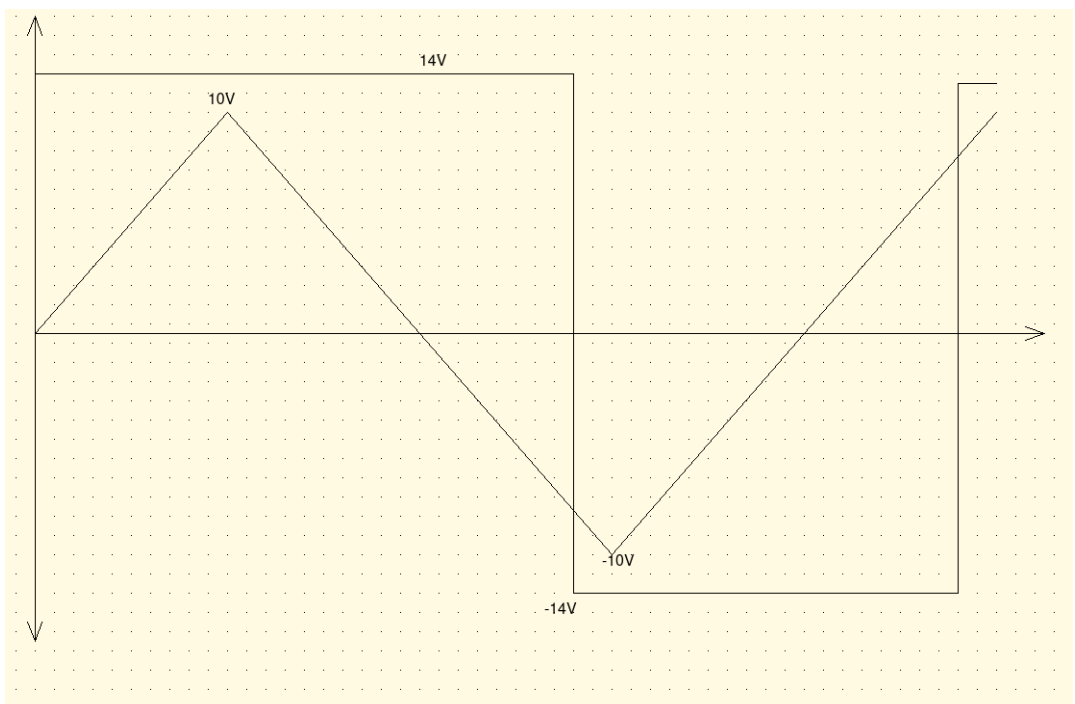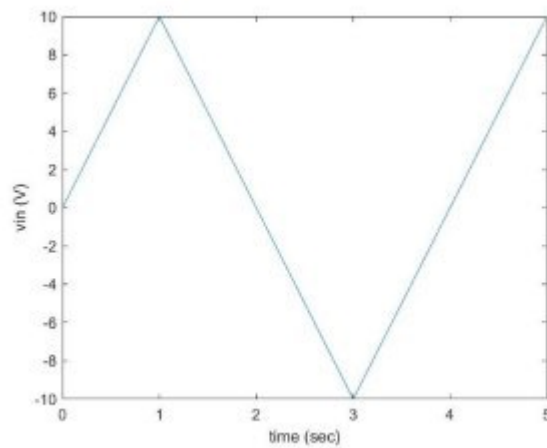

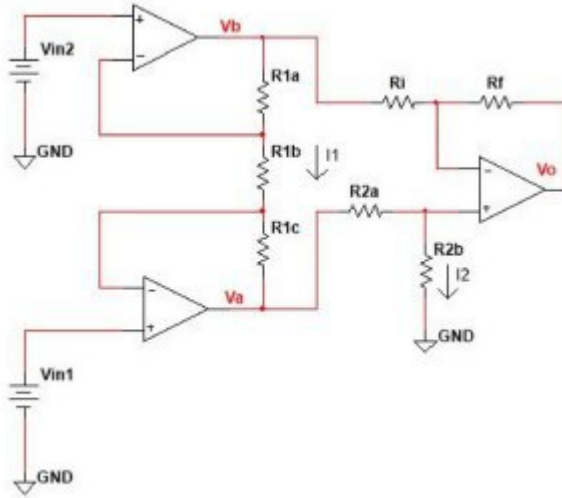16. Determine the current I_1 given all resistors are $2.0k\Omega$ except R_{1b} , which is $4.6k\Omega$, and $V_{in1} = 6V$, $V_{in2} = 13V$.



$$i_1 = \frac{v_1 - v_2}{R_{1b}} = \frac{6V - 13V}{4.6k\Omega} \quad (19)$$

$$\underline{|i_1 = 1.5mA|}$$

17. Using the same circuit and values, determine I_2 .

$$V_a = I_1(R_{1c}) = 1.52mA * 2k\Omega = 3.04V \quad (20)$$

$$3.04V + 6V = 9.04V$$

$$I = \frac{V}{R} = \frac{9.04V}{4k\Omega}$$

$$\underline{|I_2 = 2.26mA|}$$

18. A 4 pole high pass Butterworth filter has a 3dB cutoff of 6MHz. Use the image below to determine the decibel response at 2MHz.


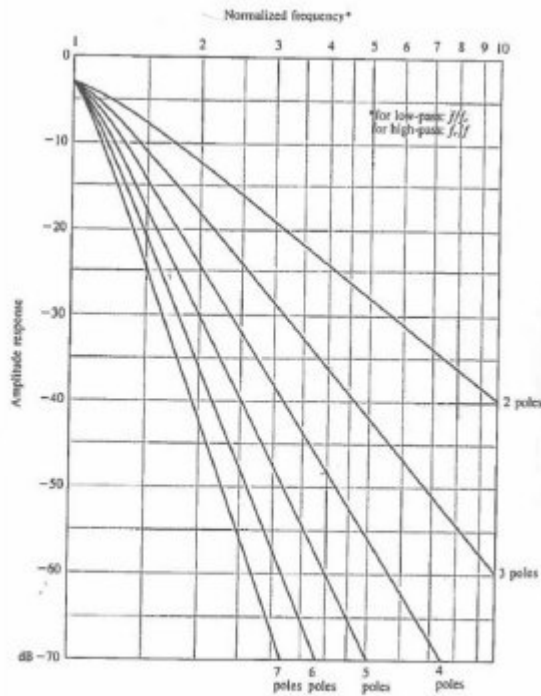


FIGURE 8-7
Stop-band amplitude response of Butterworth filters.

$$\approx -38dB \quad (21)$$

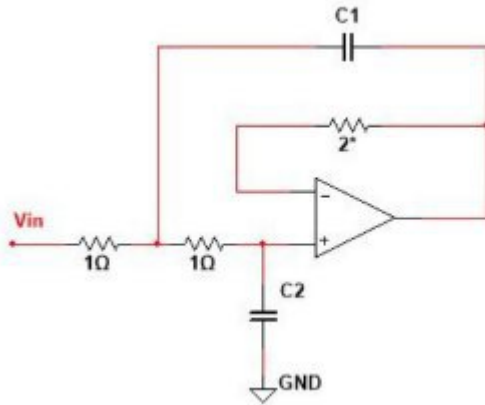19. Design a 2 pole low-pass butterworth active filter using the unity-gain amplifier (below) to achieve a 3dB frequency of 6KHz. Select the two filter resistances at $12k\Omega$ each. Starting values for C_1 and C_2 are 1.414 and 0.707 respectively.



$$R = 12k\Omega \quad (22)$$

$$C_1 = \frac{1.414F}{12k * 2 * \pi * 12k} = 1.56nF$$

$$C_1 = \frac{0.707F}{12k * 2 * \pi * 12k} = 0.78nF$$

20. What is the minimum order needed for a high pass filter that has a relative amplitude of $\leq 0.100dB$ for $f \geq 4.0kHz$, and $\geq 30.0dB$ for $f \leq 0.600kHz$.
3 poles.
21. What has been the most confusing point so far in this class?