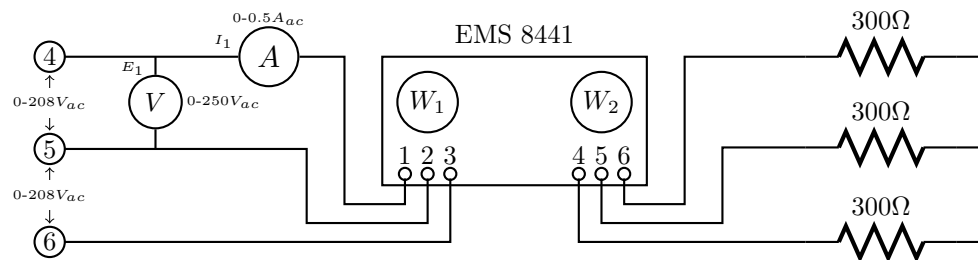


Objective

To measure power in a 3-phase circuit using 2 wattmeters and to determine the phase sequence of a 3-phase line.

Part 1

1. Connect the following circuit using the 3-phase wattmeter.



2. Turn on the power supply and adjust the line voltage to 208 VAC as indicated by E_1
3. Record the line current I_1 and the power indicated by W_1 and W_2 .

Current (A)	Power (W)	Power(W)
$I_1 =$	$W_1 =$	$W_2 =$

4. From the results of #3 calculate the 3-phase apparent power, real power, reactive power and power factor:

$S_{3\phi}$ (VA)	$P_{3\phi}$ (W)	$Q_{3\phi}$ (var)	$pf_{3\phi}$
$S_{3\phi} =$	$P_{3\phi} =$	$Q_{3\phi} =$	$pf_{3\phi} =$

5. Replace the resistance with the capacitance module. Set each capacitance to 8.8 micro Farad.
6. Repeat #2, #3 and #4.

Current (A)	Power (W)	Power(W)
$I_1 =$	$W_1 =$	$W_2 =$

$S_{3\phi}$ (VA)	$P_{3\phi}$ (W)	$Q_{3\phi}$ (var)	$pf_{3\phi}$
$S_{3\phi} =$	$P_{3\phi} =$	$Q_{3\phi} =$	$pf_{3\phi} =$


- Replace the capacitance with the inductance module. Set each inductance to 0.8 H.
- Repeat #2, #3 and #4.

Current (A)	Power (W)	Power(W)
$I_1 =$	$W_1 =$	$W_2 =$

$S_{3\phi}$ (VA)	$P_{3\phi}$ (W)	$Q_{3\phi}$ (var)	$pf_{3\phi}$
$S_{3\phi} =$	$P_{3\phi} =$	$Q_{3\phi} =$	$pf_{3\phi} =$

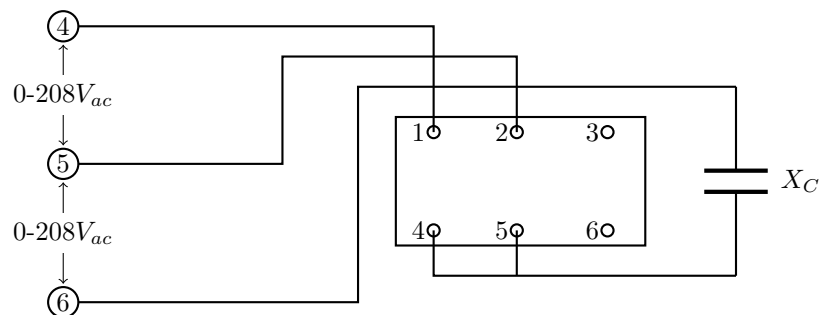Part 2

- Connect the circuit shown below using the synchronizing switch and capacitance modules.



- Set the capacitance to 2.2 uF.
- Place the synchronizing switch in its open position (to the right).
- Before turning on the power supply make sure the synchronizing switch is open!**
- Determine the phase sequence from the relative lamp brightness.
- Shut off the power supply and interchange any 2 lines.
- Turn on the power supply and adjust to 50 VAC.

8. Determine the phase sequence.
9. Replace the capacitance with the inductance module set for 3.2 H.
10. Repeat #5 and #6.
11. Write a 1 page discussion of results.

Questions

1. Could 1 wattmeter be used to measure total 3-phase power on a balanced 3-phase, 4-wire system?
2. Can a wattmeter that has I through and V across it, indicate 0 watts? Explain.
3. Could a 3-phase induction motor be used to establish the phase sequence of a 3 phase line?
4. Line voltages are 120 degrees out of phase with each other. Are the phase voltages also 120 degrees out of phase with each other? Explain.